
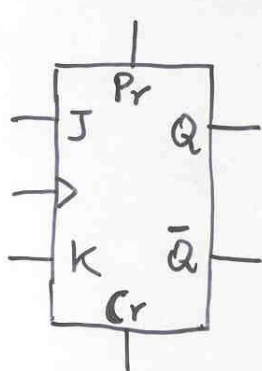


Flip-flop di tipo J-K

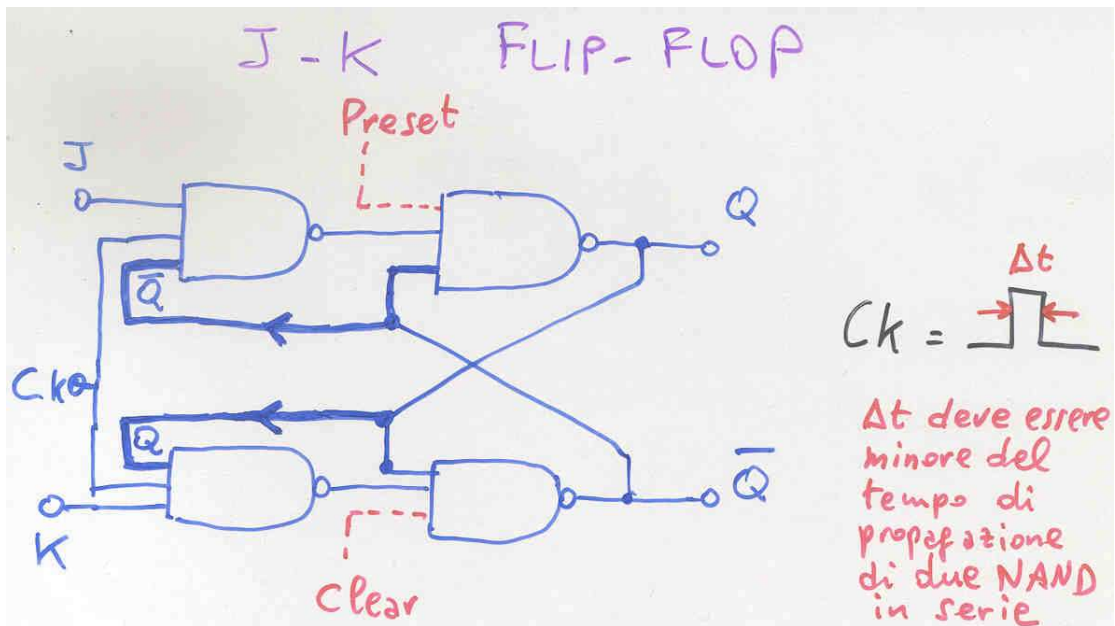

J_n	K_n	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	$\overline{Q_n}$

(assumendo $Pr = 1, Cr = 1$)

	Ck	Cr	Pr	Q
Funzionamento normale	1	1	1	* vedi ↗
Clear	0	0	1	0
Preset	0	1	0	1